

Probability Hardware Assignment


Name -: Prakhar

Roll no -: BT22BTECH11012


Abstract—In this assignment we have made a Random number generator using shift registers

PROCEDURE

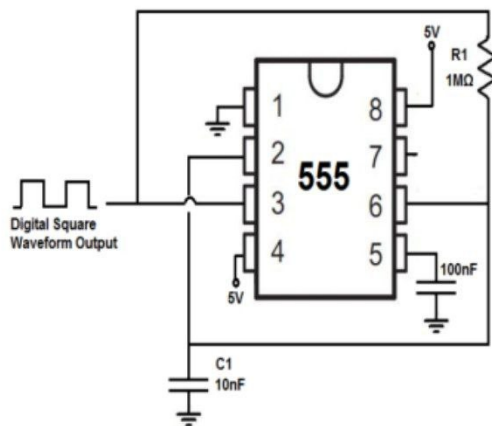
- 1) We connected the 555 timer circuit according to the figure ??



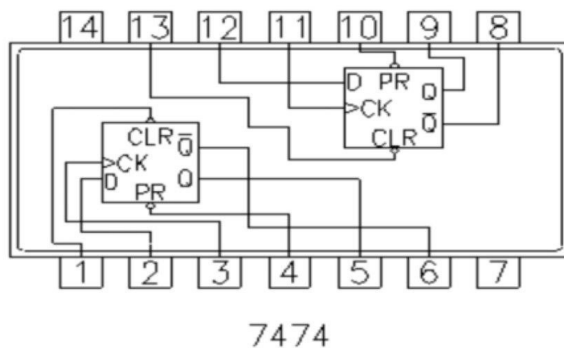- 2) Then we connected Clock output of 555 timer circuit to the clock signal of D-Flip flops
- 3) Now we make the circuit for shift registers using a 4 D-Flip flops (using two 7474 IC's)



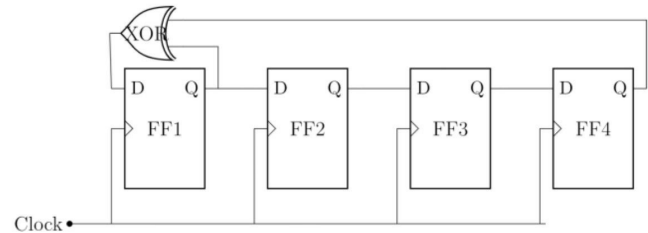- 4) Then we connected XOR gate (7486 IC) according to the figure 4
- 5) then we connected the decoder (7447 IC) and connected its A,B,C,D with Q_0, Q_1, Q_2, Q_3 respectively as per the figure 5
- 6) Then we connected The seven segmented display and then connected it with the decoder



(7447 IC) according to the table 6 and the figure 6

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

- 7) We connected all the independent parts with each other and then connected the power source

OUTPUT

Output was changing digits on the seven segment display the output is shown in figure 7

